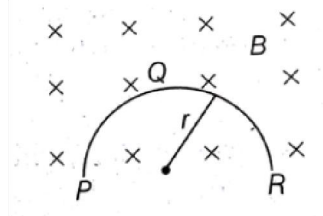


- 10) A thin semicircular conducting ring of radius 'r' is falling with its plane vertical in a horizontal magnetic induction B as shown in the figure.



The speed of the ring is 'v'. The potential difference developed across the ring is

- a) zero  
b)  $\frac{1}{2} BvR^2$   
c)  $\pi RBv$   
d)  $2RBv$
- 11) The phase difference between the alternating current and emf is  $\pi/2$ . Which of the following cannot be the constituent of the circuit?
- a) C alone  
b) L alone  
c) L,C  
d) R,L
- 12) In an LCR circuit, the voltage across each of the components L,C and R is 50V. The voltage across the LC-combination will be:
- a) 50V  
b)  $50\sqrt{2}$   
c) 100V  
d) Zero
- 13) In an LCR circuit, capacitance is changed from C to 2C. For the resonant frequency to remain unchanged, the inductance should be changed from L to:
- a) 4L  
b) 2L  
c) L/2  
d) L/4
- 14) In a series LCR circuit,  $R=200\Omega$  and the voltage and the frequency of the main supply is 220V and 50Hz respectively. On taking out the capacitor from the circuit, the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit, the current leads voltage by  $30^\circ$ . The power dissipated in the LCR circuit is
- a) zero  
b) 210W  
c) 242W  
d) 305W

